
# Ridwan Hussain & Azra Rangwala Team Azwan


#### JLab Final Project Report


### Table:


Component	Theoretical	Actual
R1	1ΜΩ	999kΩ
R2	1ΜΩ	1.00ΜΩ
R3	2.2kΩ	2.33kΩ
R4	1kΩ	945Ω
R5	1kΩ	956Ω
R6	910Ω	932Ω
R7	500Ω	539Ω
R8	560Ω	532Ω
R9	500Ω	489Ω
R11	100kΩ	100kΩ
R12	100kΩ	99.9kΩ
C1	10uF	9.123uF
C2	1nF	0.997uF
C3	68pF	67.023pF
C5	47uF	46.93uF
C6	47uF	45.17uF
L1	10uH	11.23uH

#### Simulation without Low Pass:

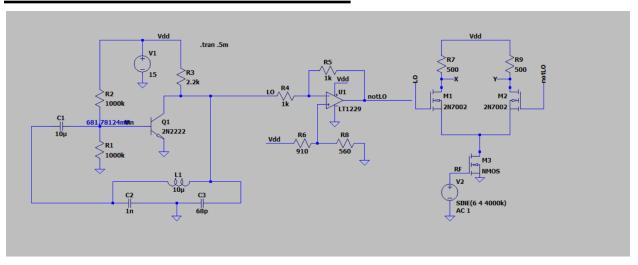

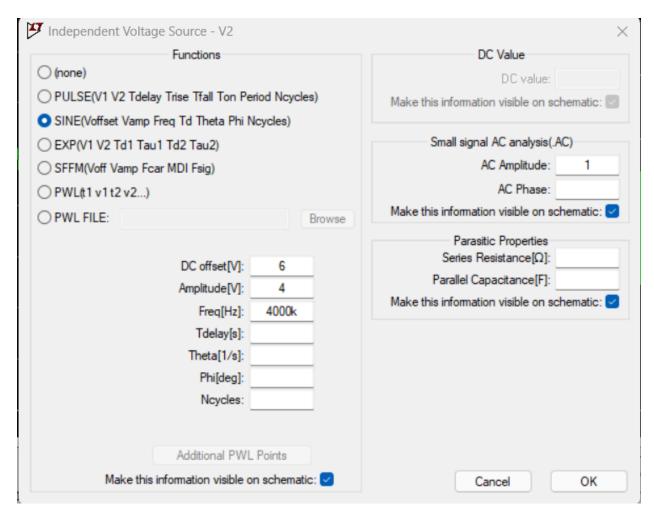

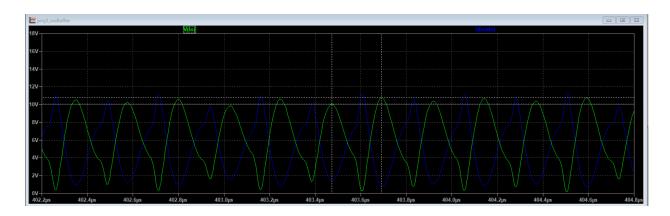


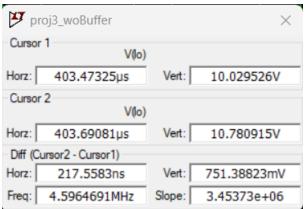




LO = 4.60 MHz, notLO = 4.45 Mhz

RF = 4000kHz = 4MHz

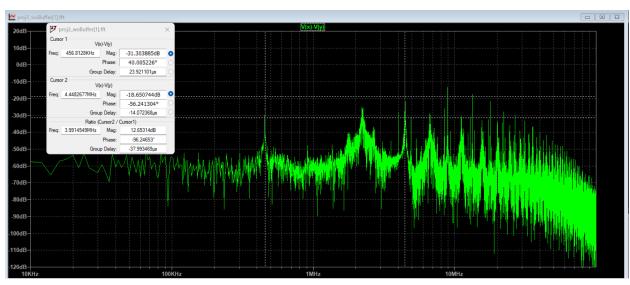


FFT Output peak at 457kHz ~ 600kHz/450kHz


# Simulation with Low Pass Filter

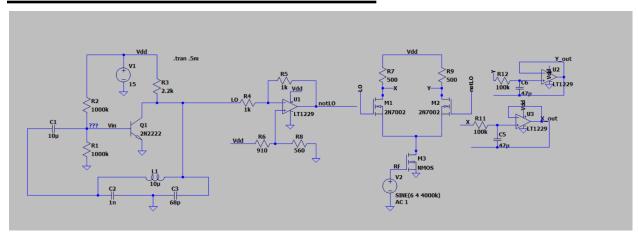

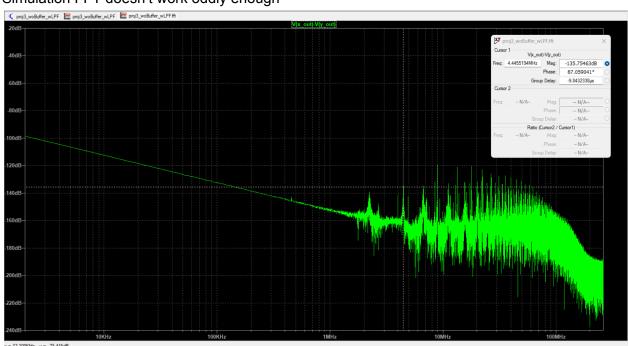
#### Simulation FFT doesn't work oddly enough



### **Actual Circuit:**

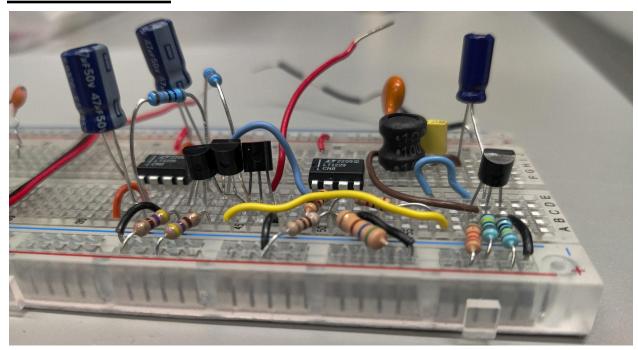
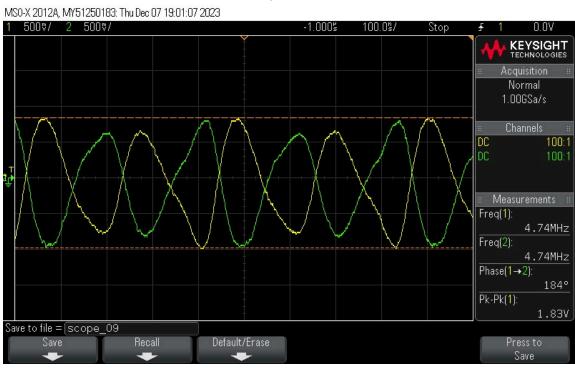
#### Phase Difference From LO (and frequency):




#### **Function Generator Parameters:**


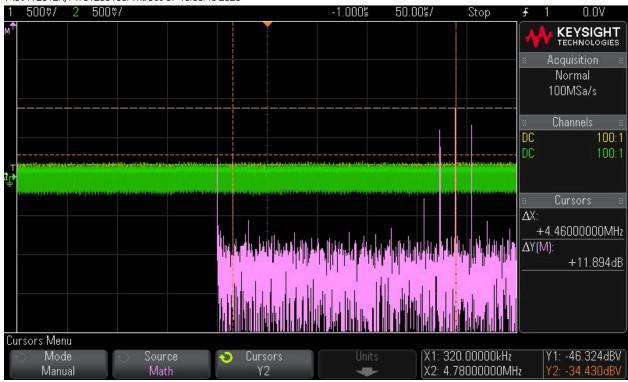
#### Active Mixer working with FFT:


MS0-X 2012A, MY51250183: Thu Dec 07 19:05:49 2023



FFT Mixer Math: RF = 5.1MHz, LO = 4.78MHz, Expected fout = 320kHz. Actual: 320kHz

# 2nd Mixing



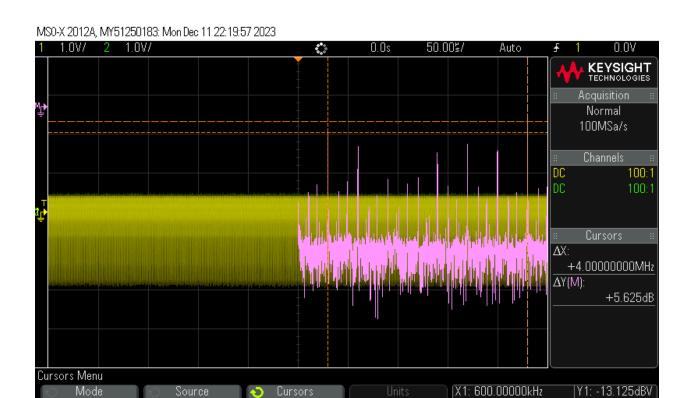

Y2: -7.500dBV

LO = 4.6MHz, RF = 4MHz. Expected fout = 600kHz. Actual fout = 600kHz

Math

Manual

## FFT Working with LPF?

